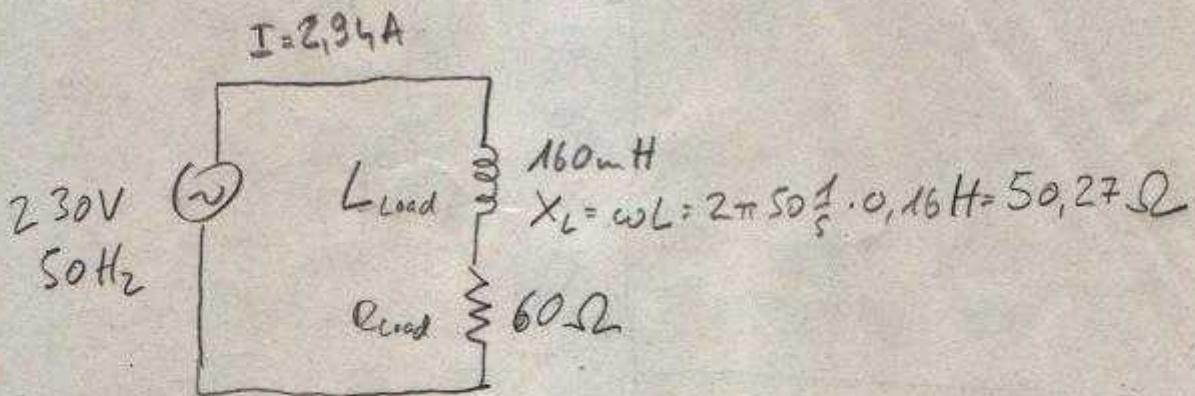


AC Lessons in electric circuits

27/8/18

Chapter 11 Power factor

$$Z = 60 \Omega + j 50,27 \Omega = 78,28 \Omega \angle 40^\circ$$


$$I = \frac{U}{Z} = \frac{230 \text{ V} \angle 0^\circ}{78,28 \Omega \angle 40^\circ} = 2,94 \text{ A} \angle -40^\circ$$

$$P = I^2 \cdot R = (2,94 \text{ A})^2 \cdot 60 \Omega = 518,62 \text{ W}$$

$$Q = I^2 \cdot X_L = (2,94 \text{ A})^2 \cdot 50,27 \Omega = 434,51 \text{ VAR}$$

$$S = U \cdot I = 230 \text{ V} \cdot 2,94 \text{ A} = 676,2 \text{ VA}$$
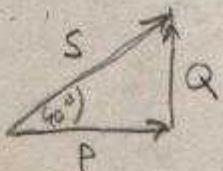
$$\text{Power factor} = \cos 40^\circ = 0,766 = \frac{P}{S}$$



27/8/18


## Power factor correction with parallel capacitor

2

$$Q = \frac{U^2}{X_C} \Rightarrow X_C = \frac{U^2}{Q} = \frac{(230V)^2}{434,51 \text{ VAR}} = 121,75 \Omega$$

$$X_C = \frac{1}{\omega C} \Rightarrow C = \frac{1}{121,75 \Omega \cdot 2\pi \cdot 50 \text{ Hz}} = 2,61 \cdot 10^{-5} \text{ F}$$

$$C = 26,1 \mu\text{F}$$

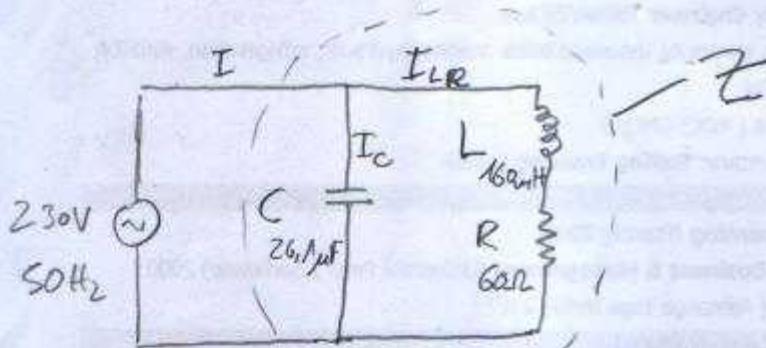

$$Z = X_C \parallel (X_L + R) = \frac{121,75 \Omega < -90^\circ \cdot 78,28 \Omega < 40^\circ}{121,75 \Omega < -90^\circ + 78,28 \Omega < 40^\circ}$$

$$Z = \frac{9530,59 \Omega^2 < -50^\circ}{0 - j121,75 \Omega + 60 \Omega + j50,27 \Omega} = \frac{9530,59 \Omega^2 < -50^\circ}{60 \Omega - j71,48 \Omega}$$


$$Z = \frac{9530,59 \Omega^2 < -50^\circ}{93,32 \Omega < -50^\circ} = 102,13 \Omega < 0^\circ$$

$$I = U / Z = 230 \text{ V} / 102,13 \Omega = 2,25 \text{ A in phase with U}$$


$$I_C = U / X_C = 230 \text{ V} / 121,75 \Omega \text{ angle } -90^\circ = 1,89 \text{ A angle } 90^\circ$$

$$I_{LR} = U / Z_{LR} = 230 \text{ V} / 78,28 \Omega \text{ angle } 40^\circ = 2,94 \text{ A angle } -40^\circ$$

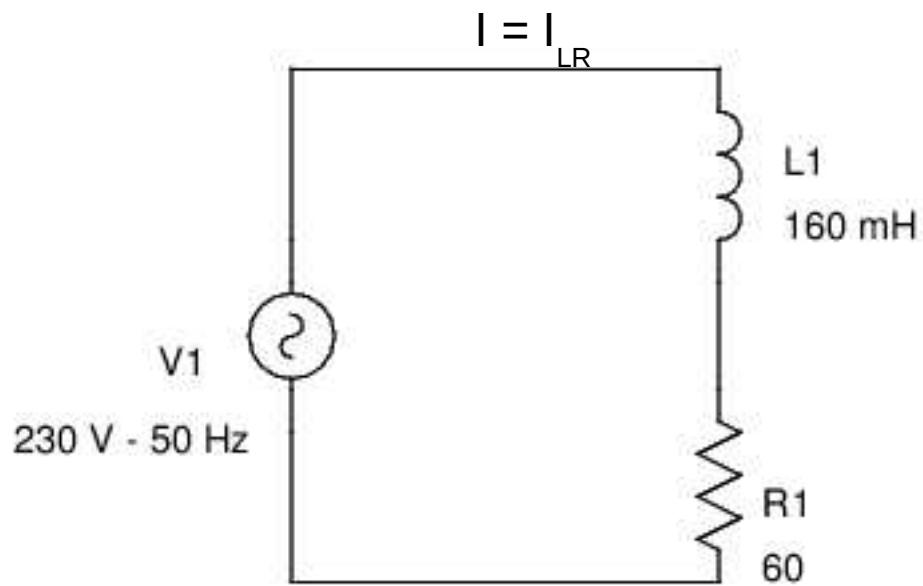Circuit without reactive power compensation  $I = 2,94 \text{ A}$



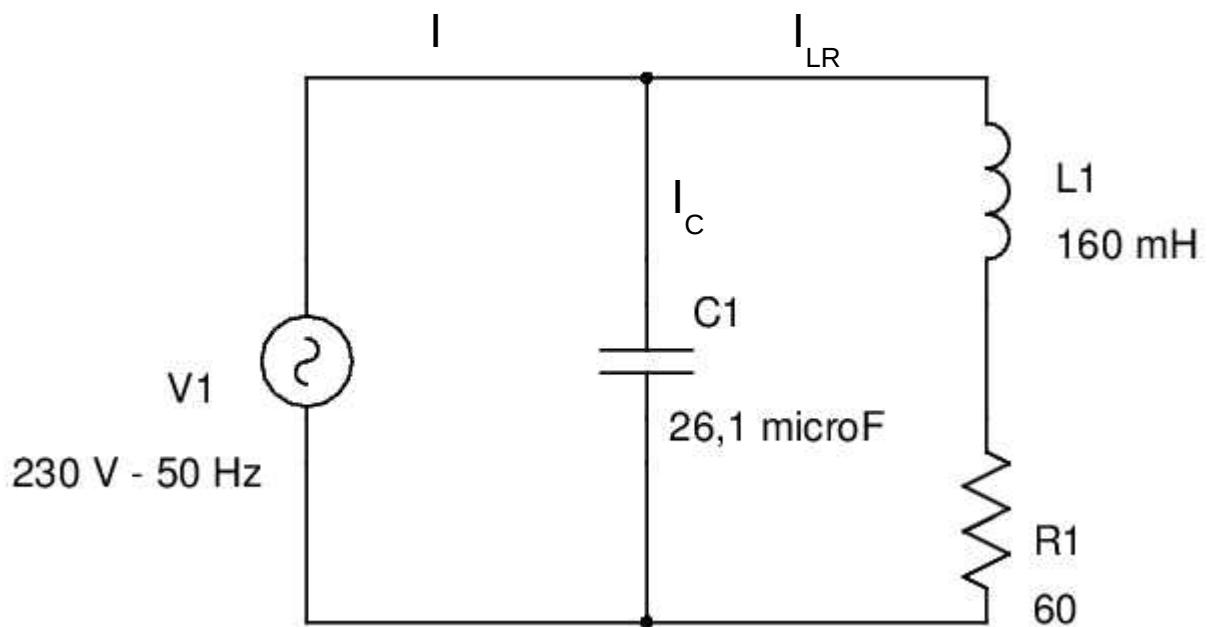Circuit with reactive power compensation  $I = 2,25 \text{ A}$



NETLIST without PF compensation

\*\*\*160 mH -- 60 ohm \*\*\*

\*Lessons in electric circuits AC - Toni Kuphaldt

\*11 Power factor

\*without Power factor compensation

vin 1 0 AC 230 sin (0 1 50); AC voltage source necessary for frequency analisys

\*inductor, the first 2 numbers are the nodes, the third the inductance in mH

I 1 2 160m

\*resistor, the first 2 numbers are the nodes, the third the resistance value in ohm

r 2 0 60

.control

\*transient analisys

\*manual 15.3.9 - tran tstep tstop <tstart <tmax>> <uic>

\* tstep time increment, 1 ms

\* tstop final time 100 ms

\* tstart start time 60 ms to observe stable behaviour after 60 ms (= 3 periods)

tran 1ms 100ms 60ms

plot v(1)

plot -vin#branch; i(t)

plot v(1, 2); vL(t)

plot v(2); vR(t)

plot v(1) -vin#branch v(1, 2)\*80 v(2)

\*frequency analisys linear one frequency from 50 Hz to 50 Hz

ac lin 1 50 50

\* v(1)- Voltage source - vm voltage magnitude and (vp angle in radians / 2pi) \* 360, converted to degrees

print v(1) vm(1) ((vp(1)/6.283)\*360)

\* v(1, 2)- Voltage over L1 - vm voltage magnitude and (vp angle in radians / 2pi) \* 360, converted to degrees

print v(1, 2) vm(1, 2) ((vp(1, 2)/6.283)\*360)

\* Total current I – rectangular coordinates

print -vin#branch;total current

\* v(2)- Voltage over R1 - vm voltage magnitude and (vp angle in radians / 2pi) \* 360, converted to degrees

print v(2) vm(2) ((vp(2)/6.283)\*360)

.endc

.end

NGSPICE simulation result NETLIST 1 without PF compensation

frequency analisys 50 Hz

Source

$v(1) = 230 \text{ V, angle } 0$

$vm(1) = 230 \text{ V, angle } 0$

L1

$v(1, 2) = 94.85 \text{ V} + j 113 \text{ V}$  (rectangular)

$vm(1, 2) = 147.70 \text{ angle } 50^\circ$  (polar)

Current I

$-vin\#branch = 2.25 \text{ A} - j 1.89 \text{ A}$  (rectangular)

$2.94 \text{ A angle } -40^\circ$  (polar)


R1

$v(2) = 135.15 \text{ V} - j 113.22 \text{ V}$  (rectangular)

$vm(2) = 176.31 \text{ V angle } -40^\circ$  (polar)

Circuit without reactive power compensation  $I = 2,94 \text{ A}$
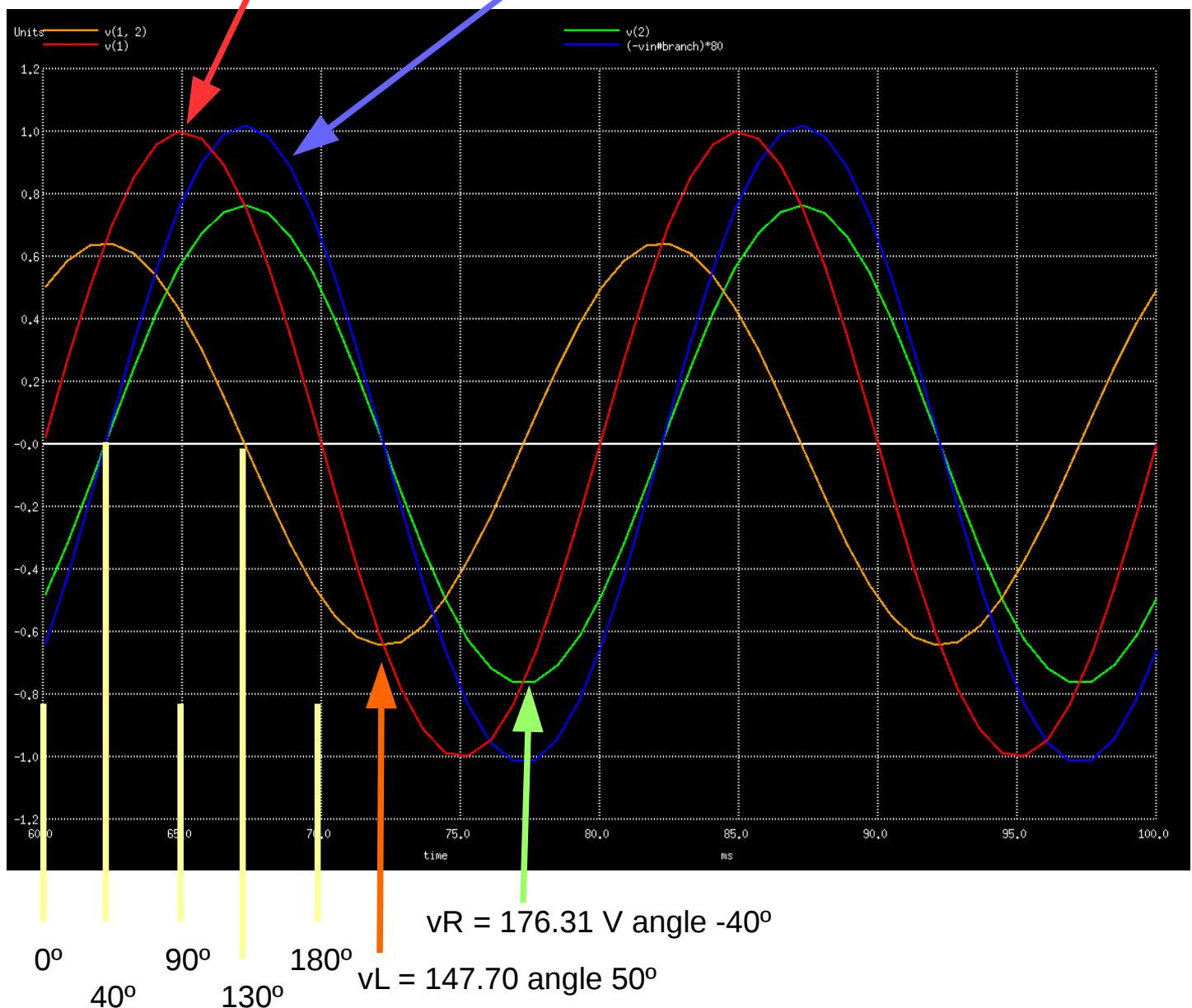
$$v_1 = v_{in} = 230 \text{ V } 50 \text{ Hz} \quad I = 2,94 \text{ A angle } -40^\circ$$



## NETLIST with PF compensation

\*\*\*160 mH -- 60 ohm // 26,1 microF \*\*\*

\*Lessons in electric circuits AC - Toni Kuphaldt

\*11 Power factor

\*Power factor compensation

\*voltage sources

vin 1 0 AC 230 sin (0 1 50); AC voltage source necessary for frequency analysys

vLR 1 2 ac 0; dummy source for C current

vC 1 4 ac 0; dummy source for C current

\*inductor, the first 2 numbers are the nodes, the third the inductance in mH

I 2 3 160m

\*resistor, the first 2 numbers are the nodes, the third the resistance value in ohm

r 3 0 60

\*capacitor, the first 2 numbers are the nodes, the third the capacitance value in microF

c 4 0 26.1u

\*\*\*\*\*

.control

\*manual 15.3.9 - tran tstep tstop <tstart <tmax>> <uic>

\* tstep time increment, 1 ms

\* tstop final time 100 ms

\* tstart start time 60 ms to observe stable behaviour after 60 ms (= 3 periods)

tran 1ms 100ms 60ms

plot v(1) (-vin#branch)\*80 v(2, 3) v(3) (vLR#branch)\*70 (vC#branch)\*60

\*frequency analysys linear one frequency from 50 Hz to 50 Hz

ac lin 1 50 50

\* v(1)- Voltage source - vm voltage magnitude and (vp angle in radians / 2pi) \* 360, converted to degrees  
print v(1) vm(1) ((vp(1)/6.283)\*360)

\* Total current I – rectangular coordinates

print -vin#branch; total current

\* v(2, 3)- Voltage over L1 - vm voltage magnitude and (vp angle in radians / 2pi) \* 360, converted to degrees  
print v(2, 3) vm(2, 3) ((vp(2, 3)/6.283)\*360)

\* v(3)- Voltage over R1 - vm voltage magnitude and (vp angle in radians / 2pi) \* 360, converted to degrees  
print v(3) vm(3) ((vp(3)/6.283)\*360)

\* Current iLR – rectangular coordinates

print vLR#branch

\* Current iC – rectangular coordinates

print vC#branch

.endc

.end

NGSPICE simulation result NETLIST 1 with PF compensation

frequency analisys 50 Hz

Source

$v(1) = 230 \text{ V, angle } 0$

$vm(1) = 230 \text{ V, angle } 0$

Current I

- $vin\#branch = 2,25 \text{ A} - j 0,0011 \text{ A}$  (rectangular)

$2,25 \text{ A angle } -0,03^\circ$  (polar)

L1

$v(2, 3) = 94.85 \text{ V} + j 113.22 \text{ V}$  (rectangular)

$vm(2, 3) = 147.70 \text{ angle } 50^\circ$  (polar)

R1

$v(2) = 135,15 \text{ V} - j 113,22 \text{ V}$  (rectangular)

$vm(2) = 176.31 \text{ V angle } -40^\circ$  (polar)

Current LR

- $vlr\#branch = 2.25 \text{ A} - j 1.89 \text{ A}$

Current C

- $vc\#branch = j 1.89 \text{ A}$

## Circuit with reactive power compensation I = 2,25 A

